
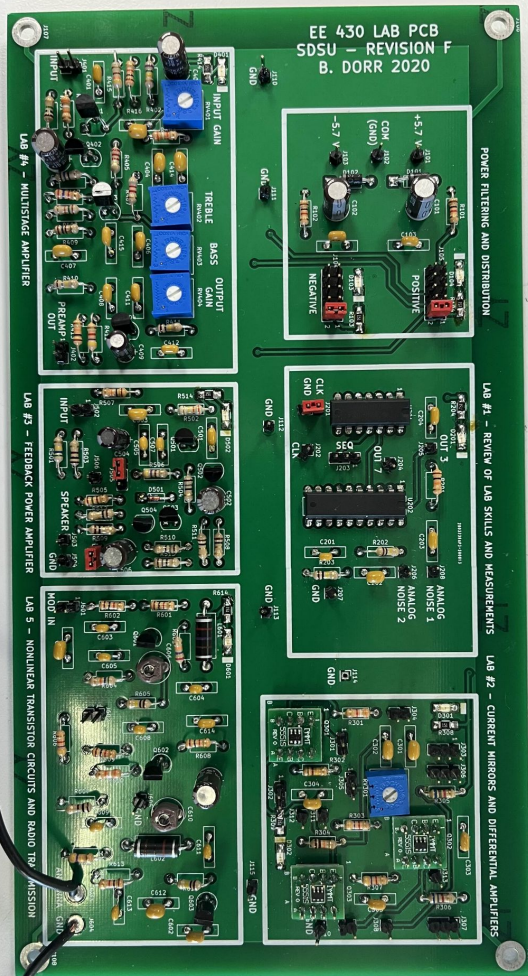


# 430L

By  
Petros Kapetanios

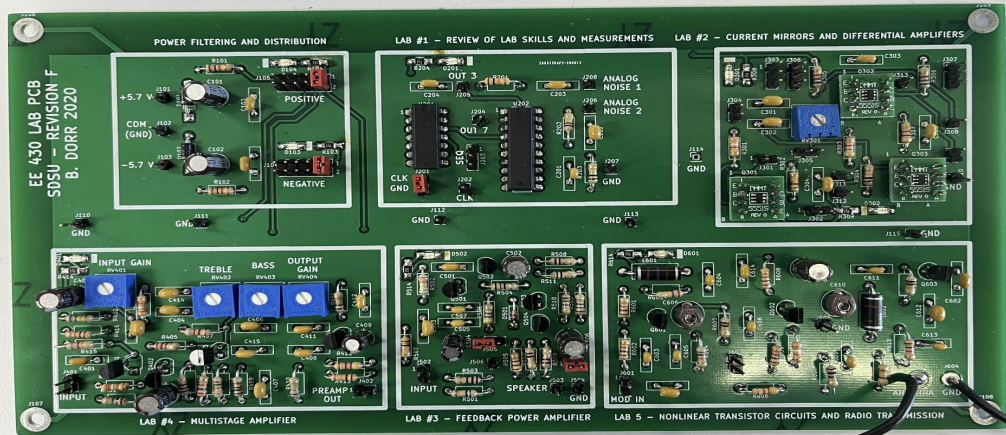





# Semester Overview



August-September

Lab 0: Filtering and Distribution

Lab 1: Review of Lab Skills and Measurements



October

Lab 2: Current Mirrors and Differential Amplifiers

Lab 3: Feedback Power Amplifier



November

Lab 3: Feedback Power Amplifier

Lab 4: Multi-Stage Amplifier



December

Lab 5: NonLinear Transistor Circuits and Radio Transmitter




# This Presentation




# Lab 2

- Current mirror and differential amplifier
- We calculated the resistance, current and beta value for this circuit with Q301
- $R_c$  refers to R301
- $R_b$  refers to R302

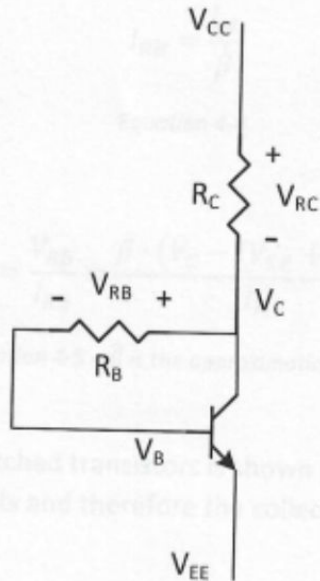

Circuit 1

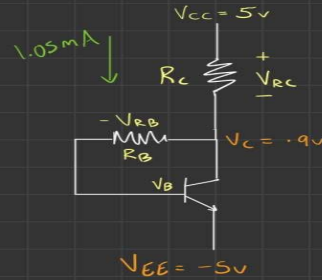

$$\frac{5 - .09}{1.05 \times 10^{-3}} = \frac{4.1}{1.03 \times 10^{-3}} \Rightarrow R_c = 3.9 \text{ k}\Omega$$

$$V_B = V_{EE} + .65 \text{ V}$$

$$V_B = -4.35 \text{ V}$$

$$R_B = \frac{.9 - (-4.35)}{10.5 \times 10^{-6}}$$

$$R_B = 500 \text{ k}\Omega$$

$$I_{RB} = \frac{I_E}{\beta} = \frac{1.05 \text{ mA}}{100} = 10.5 \mu\text{A}$$

$$\beta = \text{ideal } 100 \text{ beta that is wrong}$$

$$V_{RB} = 1.6577 \text{ V}$$

$$V_{RC} = 2.0425 \text{ V}$$



$$\beta = \frac{I_C}{I_B} \approx \frac{I_E}{I_B} = \frac{V_{RC}/R_C}{V_{RB}/R_B} = \frac{V_{RC}}{V_{RB}} \cdot \frac{R_B}{R_C}$$

$$\beta = \left( \frac{2.0425}{1.6577} \right) \left( \frac{500 \text{ k}}{3.9 \text{ k}} \right) = 157.965$$

$$\beta = 158$$



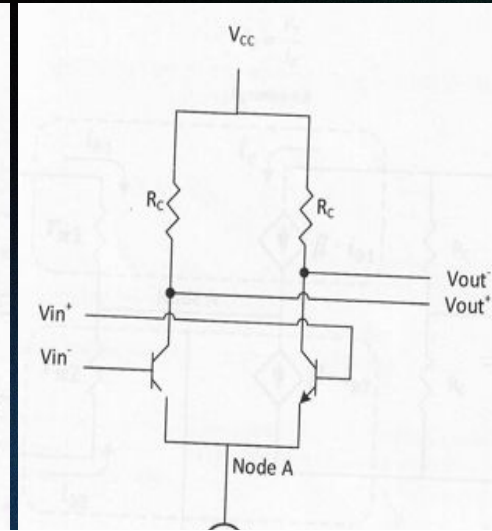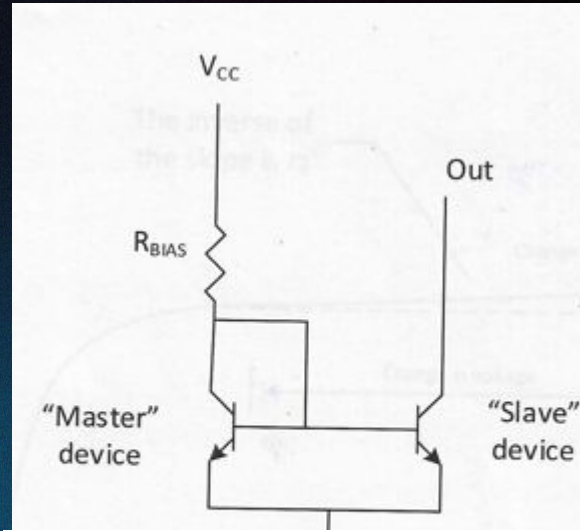- Master Device: generates the reference current
- Slave Device: replicates the reference current and outputs it
- Differential amplifier: amplifies the difference between 2 input voltages while rejecting the common voltage between them



$$A_o = 2 \cdot \frac{V_{out+}}{V_{in+}} = 2 \cdot \frac{0.8V}{13mV} = 123$$

$$A_{cm} = \frac{V_{cm out}}{V_{cm in}} = 2 \cdot \frac{20mV}{0.166V} = 0.241$$

$$CMRR = 20 \log_{10} \left( \frac{123 \cdot 0.241}{0.241} \right) = 53.1 \text{ dB}$$

- As the potentiometer is turned voltage increases but current remains moderately similar
- Our transistor had a limit of 3.7 volts so we didn't hit the rated 4.5

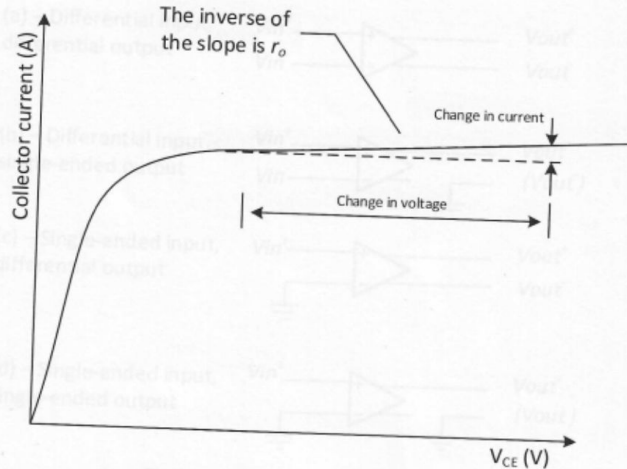


Figure 4-3 -  $r_o$  is the slope of the collector current vs  $V_{CE}$  when the transistor is in the active region.

| voltage                         | resistance     | current |
|---------------------------------|----------------|---------|
| 0.5v                            | 1.4k $\Omega$  | 0.35mA  |
| 1V                              | 2.7k $\Omega$  | 0.37mA  |
| 1.5V                            | 4.1k $\Omega$  | 0.36mA  |
| 2v                              | 5.4k $\Omega$  | 0.37mA  |
| 2.5V                            | 6.8k $\Omega$  | 0.36mA  |
| 3V                              | 8.1k $\Omega$  | 0.37mA  |
| 3.5V                            | 9.4 k $\Omega$ | 0.37mA  |
| 3.7V                            | 9.9k $\Omega$  | 0.37mA  |
| 4.5V cannot go higher than 3.7V | n/a            | n/a     |









- The amplifier can be viewed as a negative feedback control system
- The G component encompasses Q502, Q503, and Q504
- The H component focuses on the voltage divider
- The emitter of Q501 is the summing junction


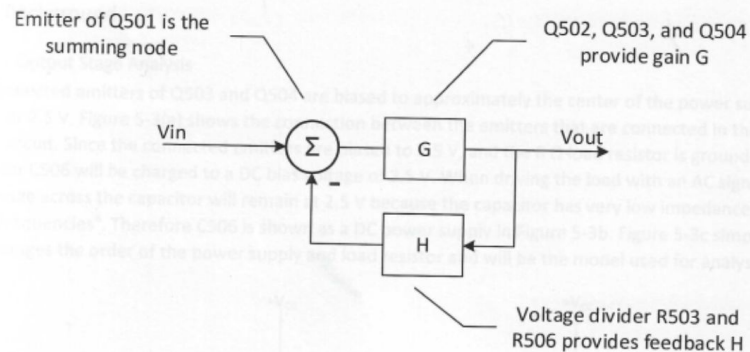


Figure 5-2 - Feedback amplifier viewed as a control system. Gain is computed for positive output signal excursions. The gain for negative excursions is identical.

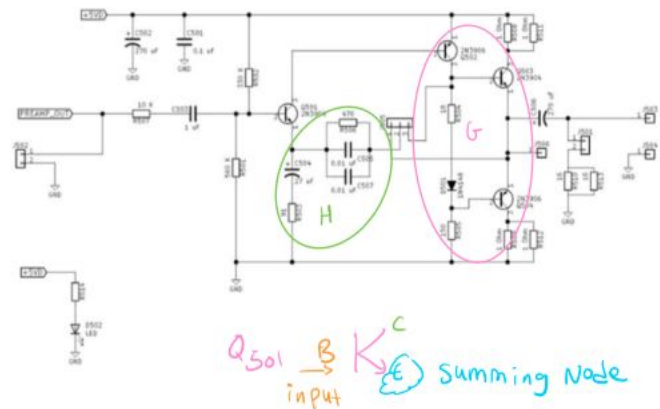







- Image 1 shows the input signal at yellow from J502, the collector at Q502 in blue, and the collector for Q503 in green
- Image 2 shows output signal of J506 in yellow, the collector of Q504 in blue, and collector of Q503 in green
- Image 3 shows the output of J503 before distortion at the 2.5 Volt peak, a 1 kHz sine wave in yellow, the collector of Q504 in blue, and the collector of Q503 in green
- Image 4 shows the output of J506, where the shorting clip was moved to produce feedback in the collector of Q502, creating a min, max, and deadzone of the transistor, the collector of Q504 in blue, and the collector of Q503 in green





## Difficulties

- In this lab we learned alternative ways of taking transistor measurements
- We learned to measure components on the same node of these transistors to measure their values



# Lab 4: Multi-Stage Amplifier

This lab consists of 4 main sections

- The input stage
- The tone stage
- Emitter follower stage
- The gain stage



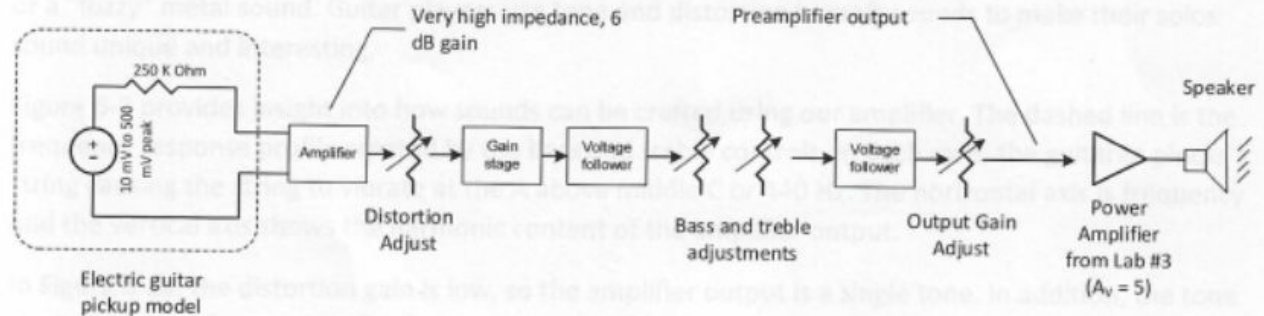


Figure 6-1 - Multistage Amplifier - Block Diagram

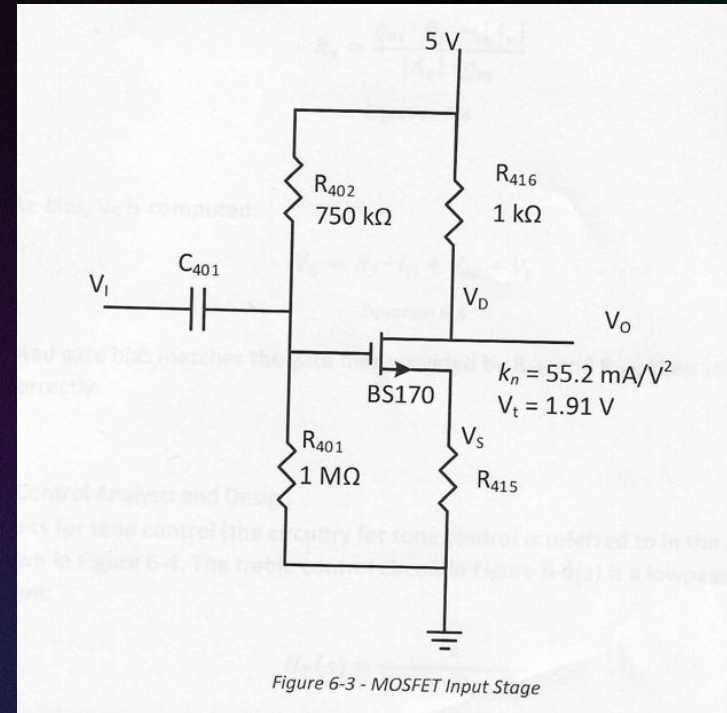
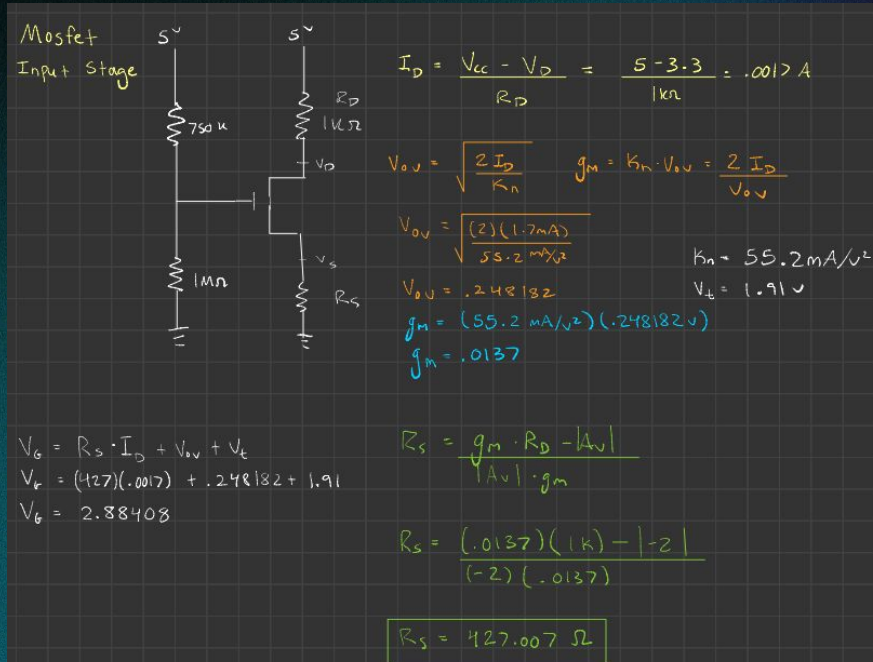
## Mosfet Input Stage

- Must have high impedance to prevent drawing current from the signal source
- The 2 bias resistors reduce the input impedance to 429 kΩ






## Tone Stack Stage


- At high frequencies CT and CB act as a short circuit (1 / 2nfc)
- Treble control from the high pass controlled by RT
- Bass control from the low pass controlled by RB

Tone Stack

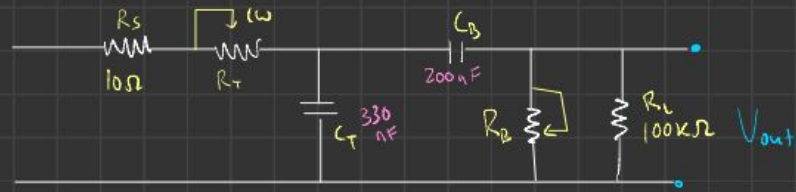

$$H_T(s) = \frac{1}{1 + s R_C C_T} \quad F_{3db} = \frac{1}{2\pi R_T C_T} \quad \text{lowpass 3db}$$
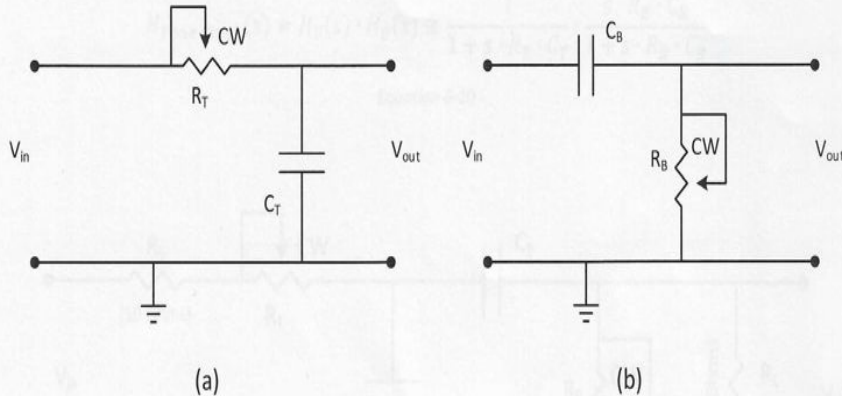
$$H_B(s) = \frac{s R_B C_B}{1 + s R_B C_B} \quad f_{3db} = \frac{1}{2\pi R_B C_B} \quad \text{High pass 3db}$$



$$482 = \frac{1}{(2\pi)(R_T)(330 \times 10^{-9})}$$

$$964 \times 10^{-6} R_T = 1$$

$$R_T = \frac{1}{964 \times 10^{-6}}$$

$$R_T = 1037.34 \Omega$$

$$88 = \frac{1}{(2\pi)(R_B)(200 \times 10^{-9})}$$

$$88 = \frac{1}{1.25663706 \times 10^{-6} R_B}$$

$$1.10584061 R_B = 1$$

$$R_B = \frac{1}{1.10584061}$$

$$R_B = 9042.895 \Omega$$

Figure 6-4 – Building blocks for Treble and Bass Tone Controls, (a) treble control, (b) bass control



## Emitter Follower

- Provides a voltage swing to the load
- Handles impedance matching for input and output
- Prevents distortion

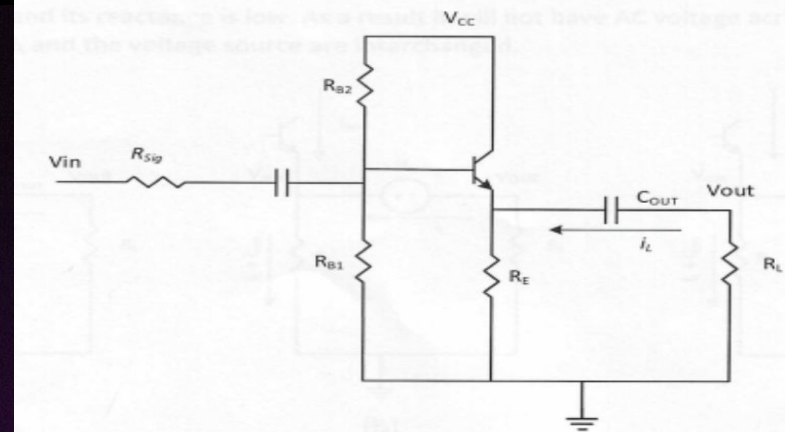



Figure 6-7 - Emitter Follower Circuit

$$r_e = \frac{V_T}{I_E} = \frac{25 \times 10^{-3}}{100 \times 10^{-6}} = 250 \Omega$$

$$r_{out} = r_e + \frac{R_{sig} \parallel R_{B1} \parallel R_{B2}}{\beta}$$

$$R_{in} = (\beta + 1)(r_e + R_E \parallel R_L)$$
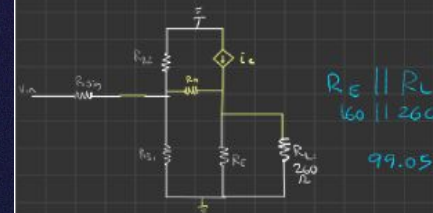
$$\begin{aligned} \beta &= 200 & R_L &= 260 \Omega \\ V_T &= 25 \text{ mV} & V_E &= 2.5 \text{ V} \\ V_{BE} &= 0.65 \text{ V} & I_{min} &= 100 \mu\text{A} \\ r_{out} &= 15 \Omega & V_{opk} &= 1.5 \text{ Vpk} \end{aligned}$$



$$R_E \parallel R_L$$

$$160 \parallel 260$$

$$99.05$$

$$V_{min} = \frac{V_{cc}}{2} - V_{opk}$$

$$\frac{V_{min}}{R_E} \geq \frac{V_{opk}}{R_L} + I_{min}$$

$$R_E \leq \frac{\frac{V_{cc}}{2} - V_{opk}}{\frac{V_{opk}}{R_L} + I_{min}}$$

$$R_E \leq \frac{\frac{5}{2} - 1.5}{\frac{1.5}{260} + 100 \mu}$$

$$R_E \leq 170.38 \Omega$$

$$R_E = 160 \Omega$$



## Gain Stage

- Determines how much voltage gain is used in the circuit
- $A_v$  of 20 is expected in an ideal case but for our circuit it is 22.4

$$C_{405} = ? \text{ from } 20\text{Hz}, \& \ 29.5\Omega$$

$$C_{405} = \frac{1}{2\pi \cdot f \cdot R} = \frac{1}{2\pi \cdot 20\text{Hz} \cdot 29.5\Omega} = 2.697 \cdot 10^{-4} \approx 270\mu\text{F}$$

$$R_E = R_{412} \parallel R_{406}, \quad g_m = \frac{I_C}{V_T}, \quad R_C = 1.5\text{k}\Omega, \quad V_C = 3.5\text{V}, \quad R_{405} = 2.2\text{k}\Omega$$

$$I_C = \frac{V_{CC} - V_C}{R_{405}} = \frac{5 - 3.5}{2.2\text{k}\Omega} = 0.682\text{mA}$$

$$g_m = \frac{0.682\text{mA}}{25\text{mV}} = 27\text{mS}$$

$$|A_v| = \frac{g_m \cdot R_C}{1 + g_m R_E} = 22.4\text{V} \Rightarrow 1 + g_m R_E = \frac{g_m R_C}{A_v} \Rightarrow g_m R_E = \frac{g_m R_C}{A_v} - 1$$

$$R_E = \frac{g_m R_C}{A_v g_m} - \frac{1}{g_m} = \frac{g_m R_C - A_v}{A_v g_m} = \frac{27\text{mS} \cdot 1.5\text{k} - 22.4}{22.4 \cdot 27\text{mS}} = 30\Omega = R_{412}$$

$$V_B = V_{CC} \cdot \frac{R_{424}}{R_{403} + R_{404}} = 5 \cdot \frac{1}{2} = 2.5\text{V} \Rightarrow V_E = V_B - V_{BE} = 2.5 - 0.65 = 1.85$$

$$I_E = \frac{V_E}{R_{406}} \Rightarrow R_{406} = \frac{V_E}{I_E} = \frac{1.85}{0.682\text{mA}} = 2.71\text{k}\Omega$$



## Difficulties

- When connecting lab 3 and lab 4, we got unusual clipping and noise
- We believed that the mosfet was the cause of the issue
- Replacing the mosfet made the signal less noisy but still led us to this abnormal signal
- Fixing 2 broken traces

